

Three Phase Alternating Current



This Power Point Presentation was created by:

Joseph David Clement Fournier B.Sc.E.E., M.Sc.E.E.
President and Senior Engineer of AscenTrust, LLC.

Website: <http://ascentrust.com>

Three Phase Alternating Current



Three-phase electric power is a common method of alternating current electric power generation, transmission, and distribution. It is a type of polyphase system and is the most common method used by electrical grids worldwide to transfer power.

It is also used to power large motors and other heavy loads.

A three-wire three-phase circuit is usually more economical than an equivalent two-wire single-phase circuit at the same line to ground voltage because it uses less conductor material to transmit a given amount of electrical power.

Three Phase Alternating Current

❖ Introduction to Faraday's Law -One



Faraday's law of induction (briefly, **Faraday's law**) is a basic law of electromagnetism predicting how a magnetic field will interact with an electric circuit to produce an electromotive force (EMF)—a phenomenon known as electromagnetic induction.

It is the fundamental operating principle of electrical generation facilities, transformers, inductors, and many types of electrical motors and solenoids.

Three Phase Alternating Current

❖ Introduction to Faraday's Law-Two




We can define a magnetic flux

$$d\Phi_B = \vec{B} \cdot d\vec{A}$$

where dA is an incremental area with the total flux being given

$$\Phi_B = \int \vec{B} \cdot d\vec{A}$$

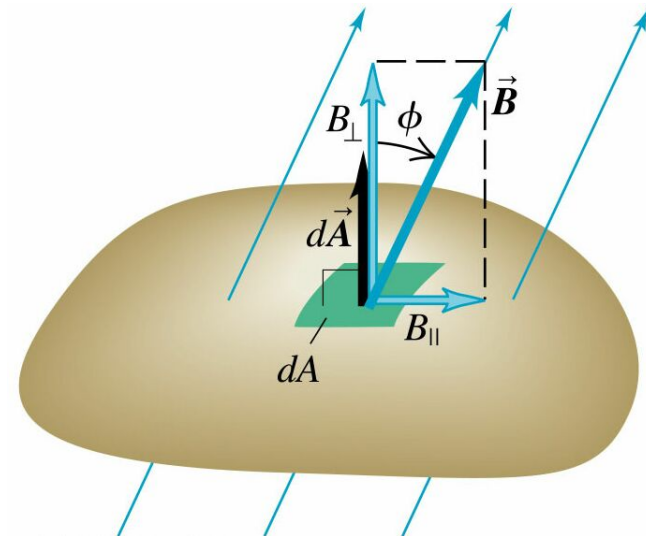Note that this integral is *not* over a closed surface, for that integral would yield zero for an answer, since there are no sources or sinks for the magnetic as there is with electric fields



Three Phase Alternating Current

❖ Introduction to Faraday's Law-Three



It was Michael Faraday who was able to link the induced current with a changing magnetic flux

He stated that:

“The induced emf (electromotive force) in a closed loop equals the negative of the time rate of change of the magnetic flux through the loop”

$$\mathcal{E} = -\frac{d\Phi_B}{dt}$$

The induced emf *opposes* the change that is occurring

Three Phase Alternating Current


❖ Introduction to Faraday's Law-Four



(Faraday's Law)

$$\mathcal{E} = -\frac{d\Phi_B}{dt} \quad (\text{Volts})$$

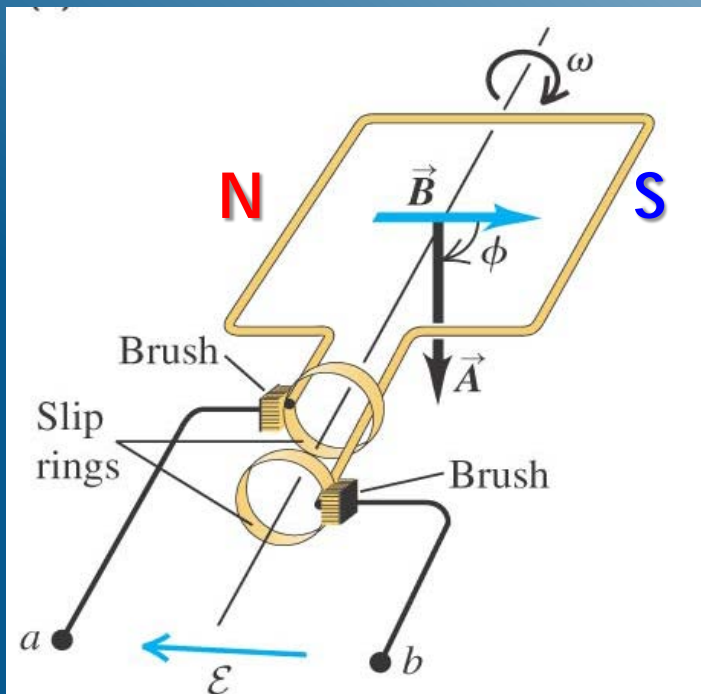- ▶ **Induced emf (electro-magnetic force)** in a closed loop equals the *negative* time rate of change of magnetic flux through the loop



$$\Phi_B = \vec{B} \cdot \vec{A} = B \cdot A \cos \phi$$


for

$$\phi = \omega t$$

$$\mathcal{E} = B \cdot A \sin \omega t$$


Three Phase Alternating Current

❖ Introduction to Faraday's Law-Five

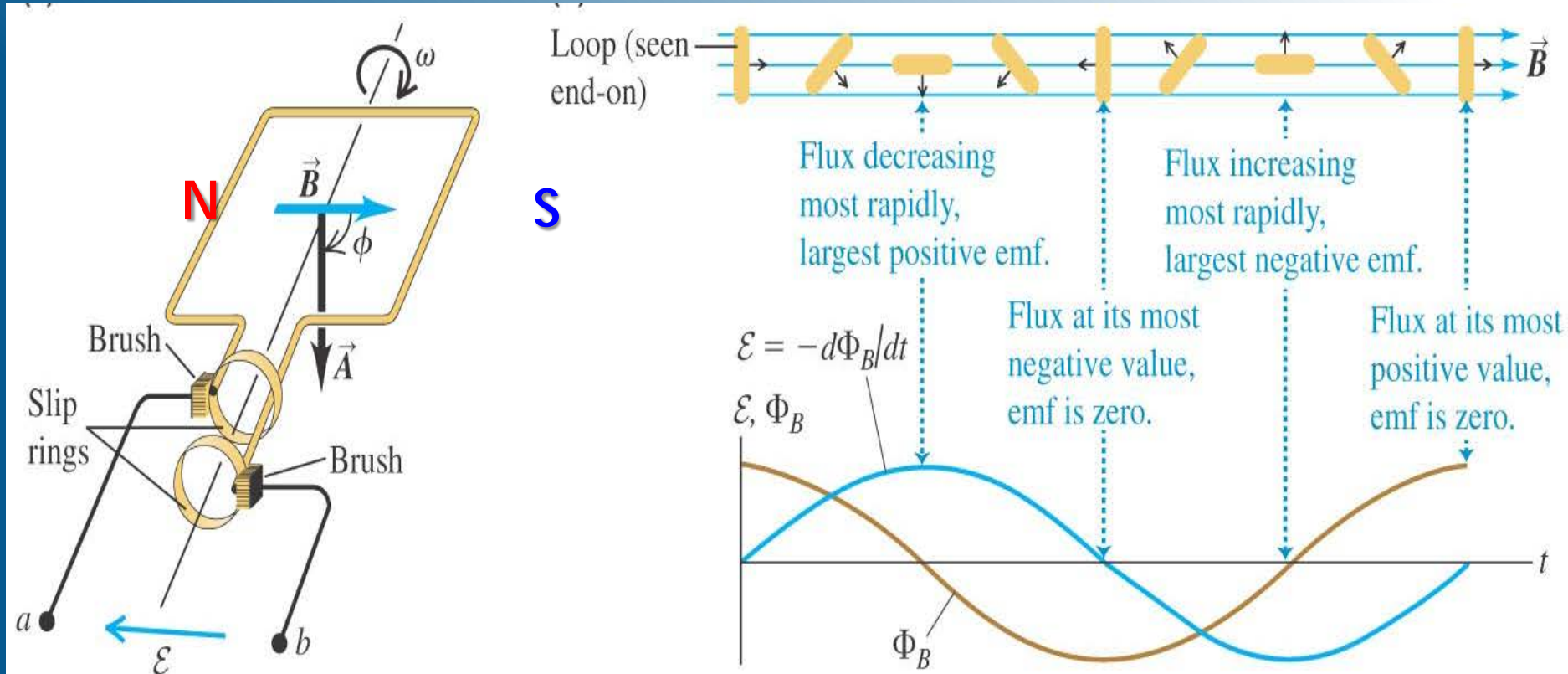

Three Phase Alternating Current


❖ Generating Three-phase Voltage

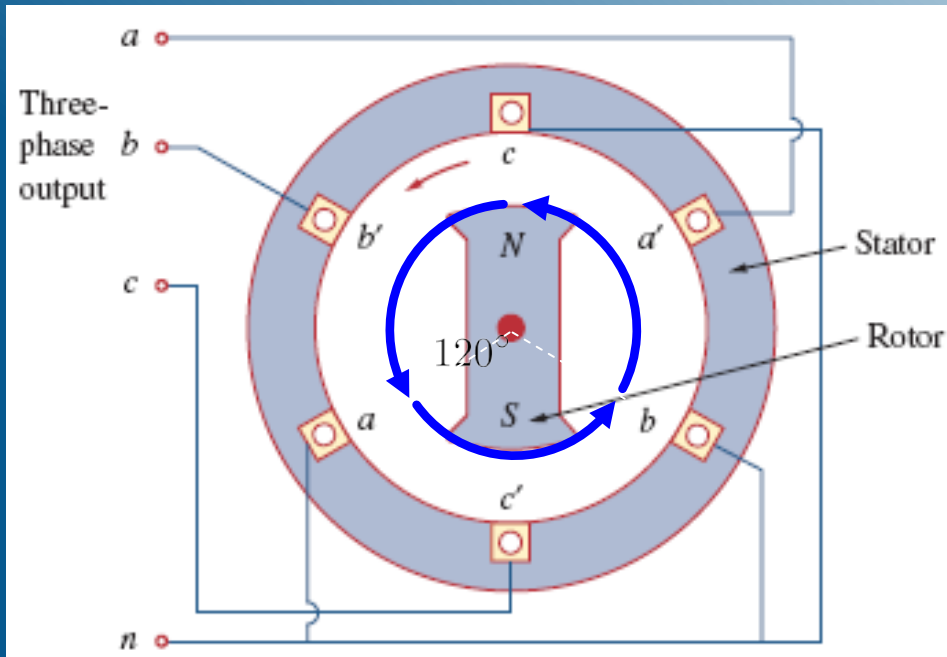


$$V_{aa'} = \sqrt{2}V \cos \omega t$$

$$V_{bb'} = \sqrt{2}V \cos(\omega t - 120^\circ)$$
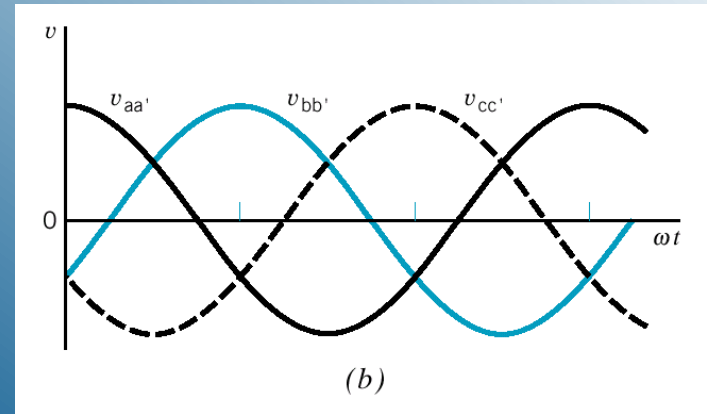
$$V_{cc'} = \sqrt{2}V \cos(\omega t - 240^\circ)$$





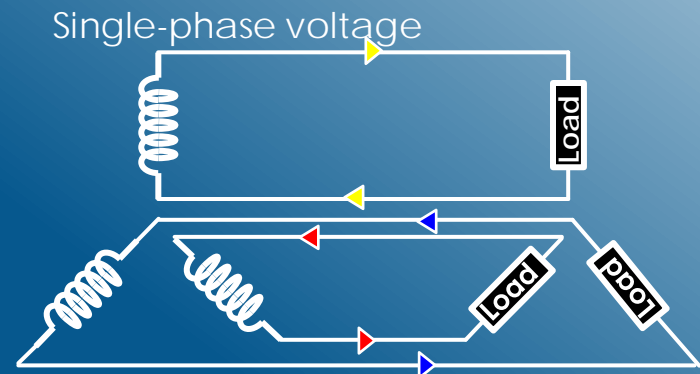- Three-phase voltage can be also generated with three single-phase voltage



Three Phase Alternating Current

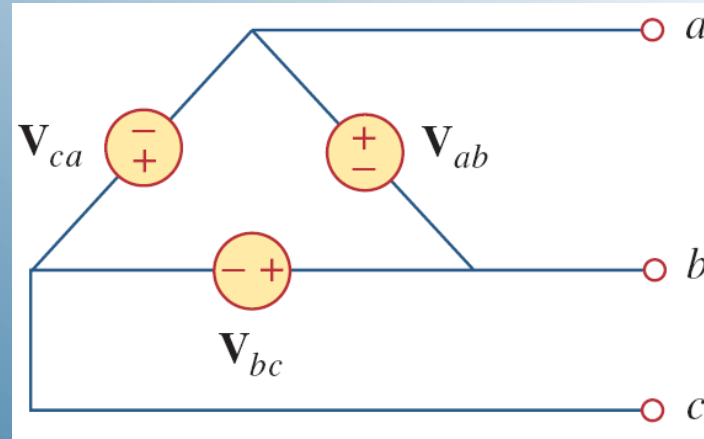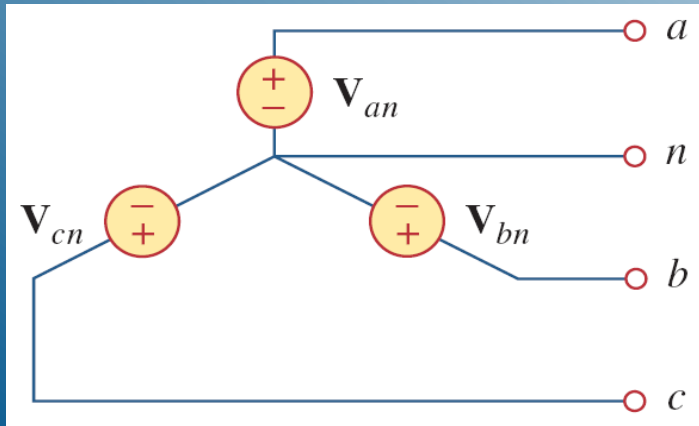- ❖ Generating Three-phase Voltage:
Two Methods of Source Connections



$$V_{an} = V_p \angle 0^\circ = V_p \cos(0^\circ) + V_p \sin(0^\circ) = V_p$$

$$V_{bn} = V_p \angle -120^\circ = V_p \cos(-120^\circ) + V_p \sin(-120^\circ) = V_p(-0.5 - 0.866j)$$

$$V_{cn} = V_p \angle -240^\circ = V_p \angle 120^\circ = V_p \cos(-240^\circ) + V_p \sin(-240^\circ) = V_p(-0.5 + 0.866j)$$

$$V_{an} + V_{bn} + V_{cn} = 0$$

⇒ voltages between the **lines a,b,c** and the **neutral line n**: **phase voltages**.

⇒ voltages between the **lines** V_{ab} , V_{bc} , V_{ca} : **phase voltages**.

Three Phase Alternating Current


❖ Phase Sequence

- Balanced phase voltages are equal in magnitude and are out of phase with each other by 120°
- There are two possible ways in which a source can be balanced

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$
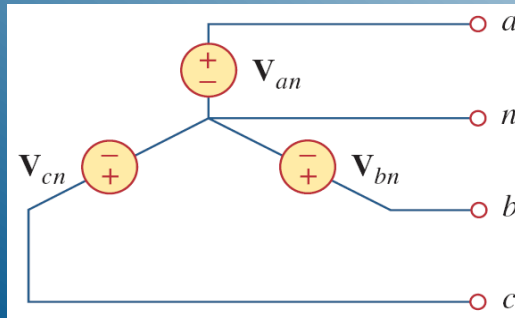
$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$



$$V_{an} = V_p \angle 0^\circ$$



$$V_{cn} = V_p \angle -120^\circ$$

$$V_{bn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$

Positive or abc sequence

The phase sequence may also be regarded as the order in which the phase voltages reach their peak (or maximum) values with respect to time.


Negative or acb sequence

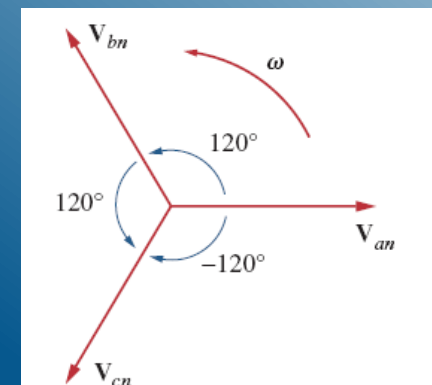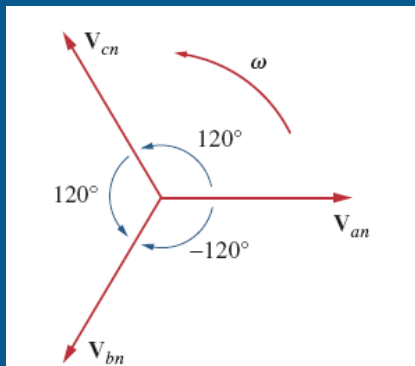

Three Phase Alternating Current

❖ Y-Delta Conversion

Y-Δ Conversion:

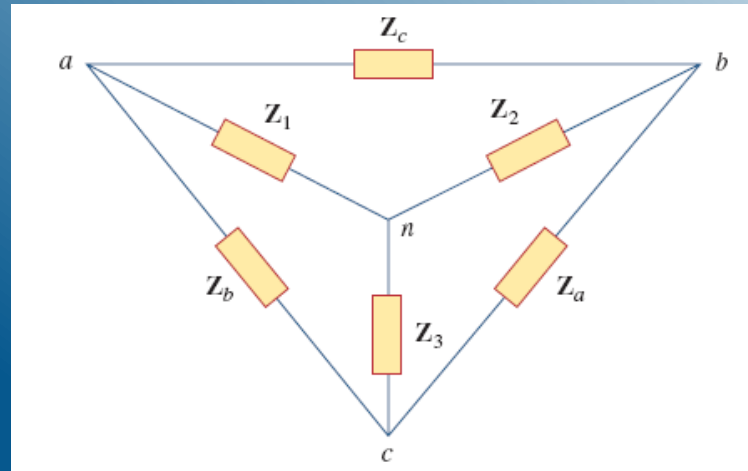

Δ-Y Conversion:

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

$$Z_{\Delta} = 3Z_Y \quad \text{or} \quad Z_Y = \frac{1}{3} Z_{\Delta}$$

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$


$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

Three Phase Alternating Current


❖ Balanced Three-phase Load

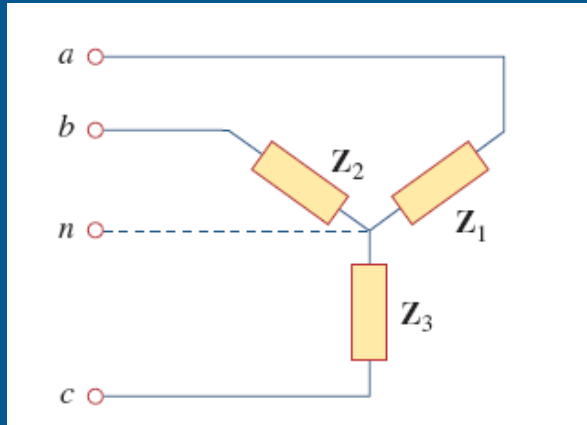- ❖ Similar to the source, the load can also be Delta or Wye connected.
- ❖ A balanced load: the phase impedances are equal in magnitude and in phase.



$$Z_1 = Z_2 = Z_3 = Z_Y$$

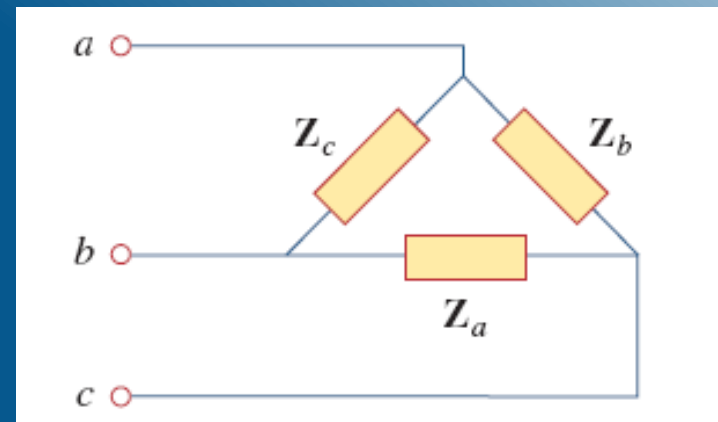
$$Z_{\Delta} = 3Z_Y \quad \text{or} \quad Z_Y = \frac{1}{3} Z_{\Delta}$$




$$Z_a = Z_b = Z_c = Z_{\Delta}$$

Three Phase Alternating Current


❖ Connections with Loads

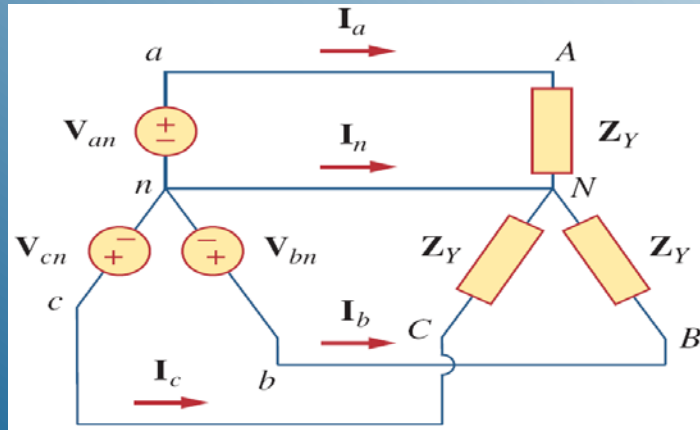


Balanced Y–Y connection

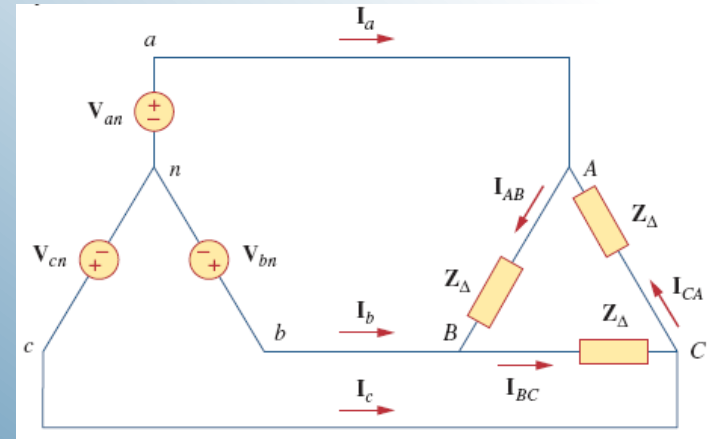

Balanced Y–Δ connection

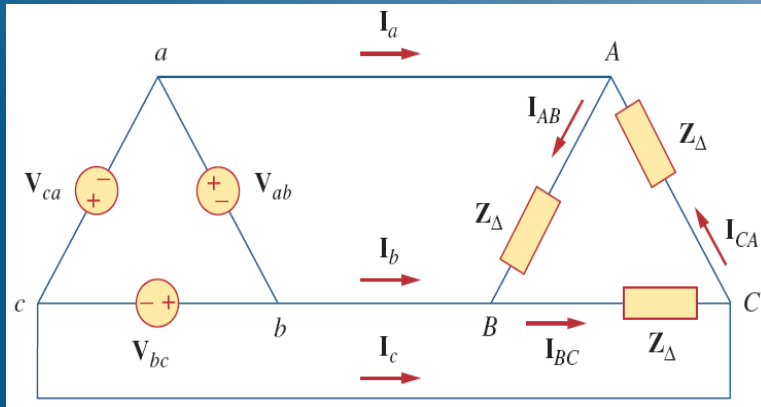


Balanced Δ–Δ connection

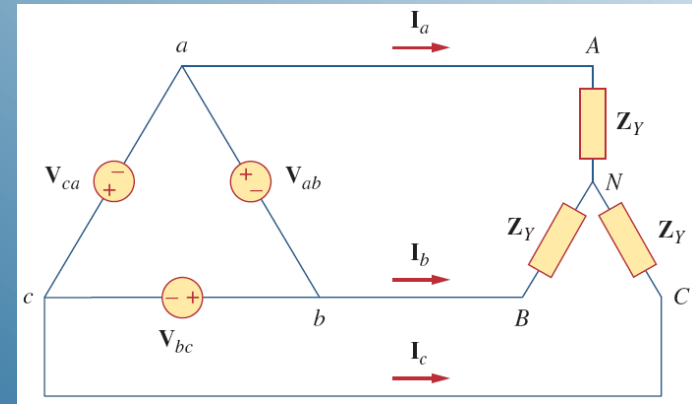

Balanced Δ–Y connection

Three Phase Alternating Current

❖ Balanced Wye-Wye Connection-One

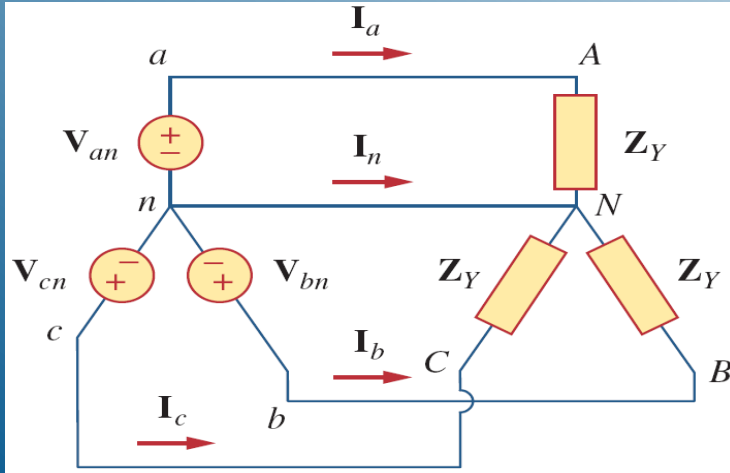


Balanced load:

$$Z_1 = Z_2 = Z_3 = Z_Y$$

Line voltage (or line-to-line voltage)

$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ \\ &= V_p \left(1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \angle 30^\circ \end{aligned}$$

Balanced Y–Y connection

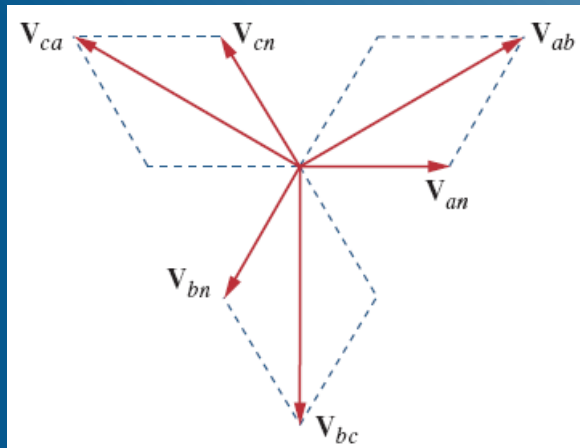


$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_p \angle -210^\circ$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_p \angle -90^\circ$$

Three Phase Alternating Current

❖ Balanced Wye-Wye Connection-Two

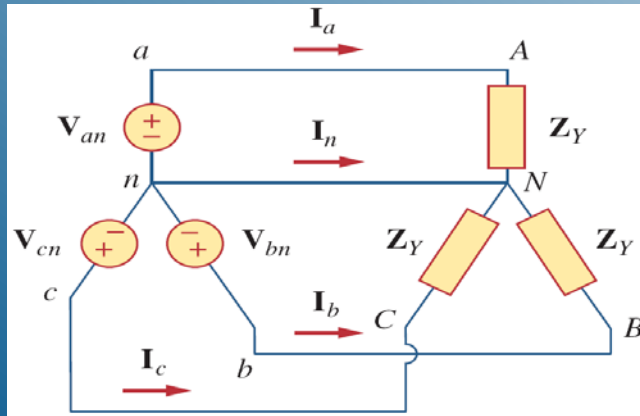

Balanced Y-Y connection

By Kirchhoff's Voltage Law (KVL), the current along the line (line current):

$$I_a = \frac{V_{an}}{Z_Y}$$

$$I_b = \frac{V_{bn}}{Z_Y} = \frac{V_{an} \angle -120^\circ}{Z_Y} = I_a \angle -120^\circ$$

$$I_c = \frac{V_{cn}}{Z_Y} = \frac{V_{an} \angle -240^\circ}{Z_Y} = I_a \angle -240^\circ$$


$$I_a + I_b + I_c = 0 \quad I_n = -(I_a + I_b + I_c) = 0 \quad V_{nN} = Z_n I_n = 0$$

Voltage across neutral line is zero: it can be removed

- Phase current is the current in each phase of the source of load.
- In Y-Y system, the line current is the same as the phase current.

Three Phase Alternating Current

❖ Balanced Wye-Delta Connection-One

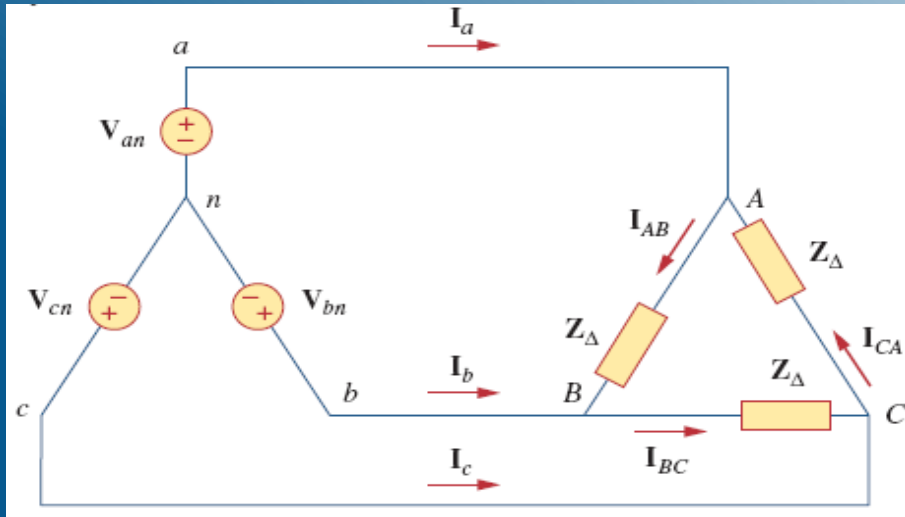

Phase voltage

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ, \quad V_{cn} = V_p \angle +120^\circ$$

Line voltage is

$$V_{ab} = V_{an} - V_{bn}$$

$$= \sqrt{3}V_p \angle 30^\circ = V_{AB}$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3}V_p \angle -90^\circ = V_{BC}$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3}V_p \angle -210^\circ$$

- Phase current can be

$$I_{AB} = \frac{V_{AB}}{Z_\Delta}, \quad I_{BC} = \frac{V_{BC}}{Z_\Delta}, \quad I_{CA} = \frac{V_{CA}}{Z_\Delta}$$


- Alternatively,

$$-V_{an} + Z_\Delta I_{AB} + V_{bn} = 0 \Rightarrow$$

$$I_{AB} = \frac{V_{an} - V_{bn}}{Z_\Delta} = \frac{V_{ab}}{Z_\Delta} = \frac{V_{AB}}{Z_\Delta}$$

Three Phase Alternating Current

❖ Balanced Wye-Delta Connection-Two

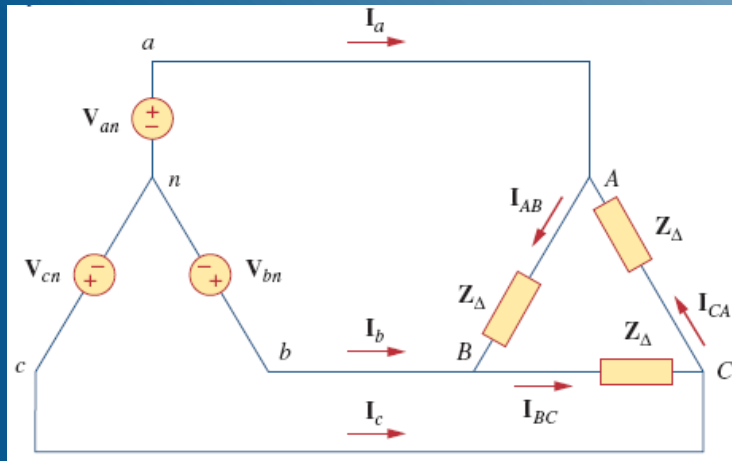

- Line currents are obtained by KCL


$$\begin{aligned} I_a &= I_{AB} - I_{CA} = I_{AB}(1 - 1 \angle -240^\circ) \\ &= I_{AB}(1 + 0.5 - j0.866) = I_{AB} \sqrt{3} \angle -30^\circ \end{aligned}$$

$$I_b = I_{BC} - I_{AB}, \quad I_c = I_{CA} - I_{BC}$$

- Magnitude of line currents:


$$I_L = \sqrt{3} I_p$$

$$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

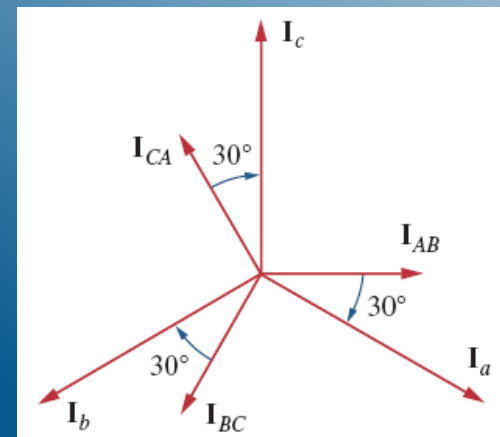

Three Phase Alternating Current

❖ Balanced Delta-Delta Connection-One

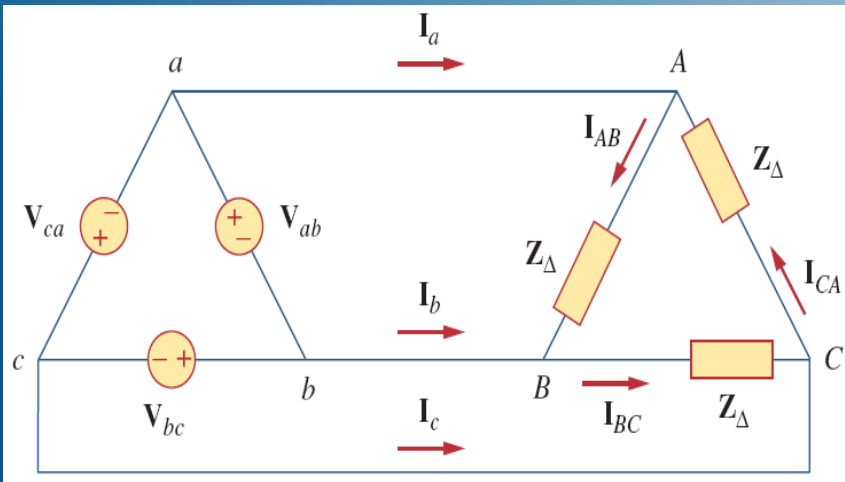

Assuming a positive sequence, the phase voltages for a delta-connected source are

$$\underline{V}_{ab} = V_p \angle 0^\circ \quad \underline{V}_{bc} = V_p \angle -120^\circ \quad \underline{V}_{ca} = V_p \angle +120^\circ$$

⇒ The line voltages are the same as the phase voltage

The phase currents

$$\underline{V}_{ab} = \underline{V}_{AB}, \quad \underline{V}_{bc} = \underline{V}_{BC}, \quad \underline{V}_{ca} = \underline{V}_{CA}$$


$$\underline{I}_{AB} = \frac{\underline{V}_{AB}}{Z_\Delta} = \frac{\underline{V}_{ab}}{Z_\Delta} \quad \underline{I}_{BC} = \frac{\underline{V}_{BC}}{Z_\Delta} = \frac{\underline{V}_{bc}}{Z_\Delta} \quad \underline{I}_{CA} = \frac{\underline{V}_{CA}}{Z_\Delta} = \frac{\underline{V}_{ca}}{Z_\Delta}$$

The line currents are obtained from the phase currents by applying KCL at nodes A, B, and C

$$\underline{I}_c = \underline{I}_{CA} - \underline{I}_{BC} \quad \underline{I}_b = \underline{I}_{BC} - \underline{I}_{AB} \quad \underline{I}_a = \underline{I}_{AB} - \underline{I}_{CA}$$

Three Phase Alternating Current

❖ Balanced Delta-Wye Connection

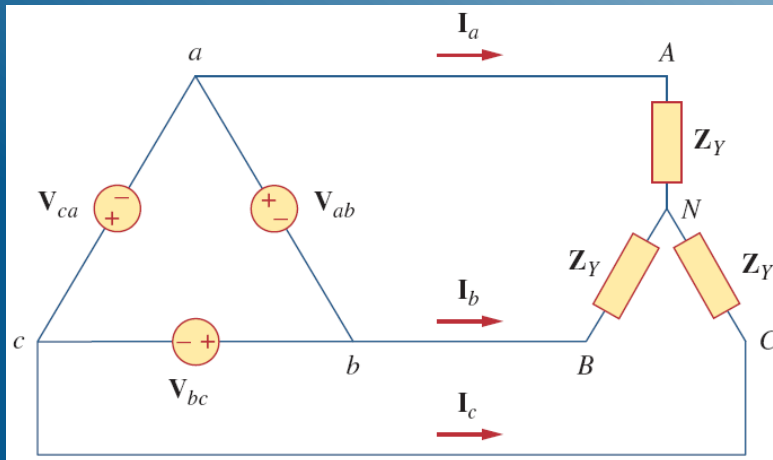

Assuming the *abc* sequence, the phase voltages of a delta-connected source are

These are also the line voltages as well as the phase voltages.

$$\mathbf{V}_{ab} = V_p \angle 0^\circ$$

$$\mathbf{V}_{bc} = V_p \angle -120^\circ$$

$$\mathbf{V}_{ca} = V_p \angle +120^\circ$$

In order to get the line current, apply KVL to loop *aANBba*,

$$-\mathbf{V}_{ab} + \mathbf{Z}_Y \mathbf{I}_a - \mathbf{Z}_Y \mathbf{I}_b = 0$$

$$\Rightarrow \mathbf{Z}_Y (\mathbf{I}_a - \mathbf{I}_b) = \mathbf{V}_{ab} = V_p \angle 0^\circ$$



$$\Rightarrow \mathbf{I}_a - \mathbf{I}_b = \frac{V_p \angle 0^\circ}{\mathbf{Z}_Y}$$

\mathbf{I}_b lags \mathbf{I}_a by 120° , since we assumed the *abc* sequence.

Three Phase Alternating Current

❖ Delta-Wye Transformation

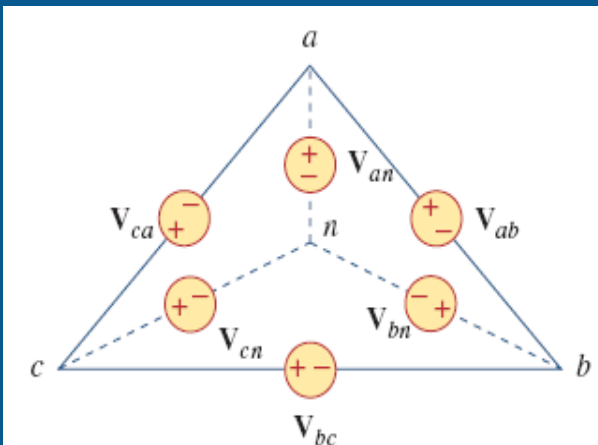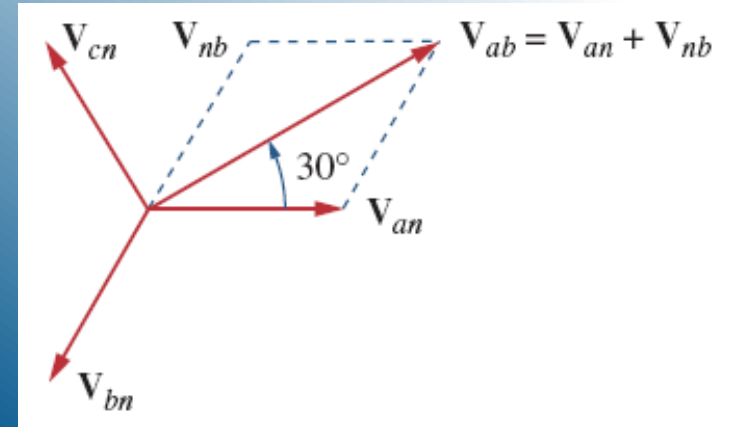- ❖ Another possible way to analyze the Delta-Star connection.
 - ❖ Transform Delta connected source to Star connected source
 - ❖ Analyze the Y-Y connection.
- ❖ Observing the phase voltage to line voltage relation in the Y-Y connection



$$V_{ab} = V_p \angle 0^\circ, \quad V_{bc} = V_p \angle -120^\circ$$

$$V_{ca} = V_p \angle +120^\circ$$

$$V_{an} = \frac{V_p}{\sqrt{3}} \angle -30^\circ$$

$$V_{bn} = \frac{V_p}{\sqrt{3}} \angle -150^\circ, \quad V_{cn} = \frac{V_p}{\sqrt{3}} \angle +90^\circ$$

Three Phase Alternating Current

❖ Power in a Balanced System-One



For a Y-connected load, the phase voltages are

(V_p (rms) of the phase voltage)

$$v_{AN} = \sqrt{2}V_p \cos \omega t$$

$$v_{BN} = \sqrt{2}V_p \cos(\omega t - 120^\circ)$$

$$v_{CN} = \sqrt{2}V_p \cos(\omega t + 120^\circ)$$

If $\mathbf{Z}_Y = Z/\theta$,

the phase currents lag behind their corresponding phase voltages by θ

$$i_a = \sqrt{2}I_p \cos(\omega t - \theta)$$

$$i_b = \sqrt{2}I_p \cos(\omega t - \theta - 120^\circ)$$

$$i_c = \sqrt{2}I_p \cos(\omega t - \theta + 120^\circ)$$

The total instantaneous power in the load is the sum of the instantaneous powers in the three phases

$$\begin{aligned} p &= p_a + p_b + p_c = v_{AN}i_a + v_{BN}i_b + v_{CN}i_c \\ &= 2V_p I_p [\cos \omega t \cos(\omega t - \theta) + \cos(\omega t - 120^\circ) \cos(\omega t - \theta - 120^\circ) + \cos(\omega t + 120^\circ) \cos(\omega t - \theta + 120^\circ)] \end{aligned}$$

Three Phase Alternating Current

❖ Power in a Balanced System-Two



Applying the trigonometric identity,

$$\cos A \cos B = \frac{1}{2}[\cos(A + B) + \cos(A - B)]$$

$$\begin{aligned} p &= V_p I_p [3 \cos \theta + \cos(2\omega t - \theta) + \cos(2\omega t - \theta - 240^\circ) \\ &\quad + \cos(2\omega t - \theta + 240^\circ)] \\ &= V_p I_p [3 \cos \theta + \cos \alpha + \cos \alpha \cos 240^\circ + \sin \alpha \sin 240^\circ \\ &\quad + \cos \alpha \cos 240^\circ - \sin \alpha \sin 240^\circ] \\ &\quad \text{where } \alpha = 2\omega t - \theta \\ &= V_p I_p \left[3 \cos \theta + \cos \alpha + 2 \left(-\frac{1}{2} \right) \cos \alpha \right] = 3V_p I_p \cos \theta \end{aligned}$$

Thus the total instantaneous power in a balanced three-phase system is constant—it does not change with time as the instantaneous power of each phase does.

Three Phase Alternating Current

❖ Power in a Balanced System-Three



Average power per phase for either the Δ -connected load or the Y-connected load is $p/3$, or

$$P_p = V_p I_p \cos \theta$$

The reactive power per phase

$$Q_p = V_p I_p \sin \theta$$

The apparent power per phase

$$S_p = V_p I_p$$

The complex power per phase

$$\mathbf{S}_p = P_p + jQ_p = \mathbf{V}_p \mathbf{I}_p^*$$

Three Phase Alternating Current

❖ Power in a Balanced System-Four



The total average power is the sum of the average powers in the phases

$$P = P_a + P_b + P_c = 3P_p = 3V_p I_p \cos\theta = \sqrt{3}V_L I_L \cos\theta$$

The total reactive power

$$Q = 3V_p I_p \sin\theta = 3Q_p = \sqrt{3}V_L I_L \sin\theta$$

The total complex power

$$\mathbf{S} = 3\mathbf{S}_p = 3\mathbf{V}_p \mathbf{I}_p^* = 3I_p^2 \mathbf{Z}_p = \frac{3V_p^2}{\mathbf{Z}_p^*}$$

where $\mathbf{Z}_p = Z_p/\theta$ is the load impedance per phase.

$$\mathbf{S} = P + jQ = \sqrt{3}V_L I_L \underline{\theta}$$

Three Phase Alternating Current

❖ Advantage of three-phase Circuit



- ▶ Consider an amount of power P_L being transmitted at the same line voltage V_L using

- ▶ Single phase supply
- ▶ 3-phase balanced supply

- ▶ Power dissipation in transmission

$$I_L = \frac{P_L}{V_L}$$

$$P_{loss} = 2I_L^2 R = 2R \frac{P_L^2}{V_L^2}$$

$$I'_L = |\mathbf{I}_a| = |\mathbf{I}_b| = |\mathbf{I}_c| = P_L / (\sqrt{3}V_L)$$

$$P'_{loss} = 3(I'_L)^2 R' = 3R' \frac{P_L^2}{3V_L^2} = R' \frac{P_L^2}{V_L^2}$$

$$I'_L = |\mathbf{I}_a| = |\mathbf{I}_b| = |\mathbf{I}_c| = P_L / (\sqrt{3}V_L)$$

$$P'_{loss} = 3(I'_L)^2 R' = 3R' \frac{P_L^2}{3V_L^2} = R' \frac{P_L^2}{V_L^2}$$

